 


Struktury počítačových systémů

Přednáší: Richard Šusta

20. října 2011 verze 1.0




ČVUT-FEL v Praze – kód předmětu A0B35SPS

Graphic/Memory Arrays

...and their addressing

Reading/writing data matrices

 - direct addressing - e.g. 7 segment, CRT
- shift registers - e.g. CCD
- row/column - e.g. LCD, memories




SPS

3

Method-1: Direct addressing

Pixel are connected by direct wires

 


SPS

4

Method-1: Cathode Ray Tubes

 - Direct addressing by deflected electron beam




SPS

5

Raster Scan

deflection - cz: vychylování

 

The beam is off during retrace.

Horizontal - beam returns to left edge

Vertical - beam returns to upper left corner.

Interlaced monitor scans odd lines in odd pictures and even lines in even pictures



CRT display

Active lines


Retrace lines

SPS

6

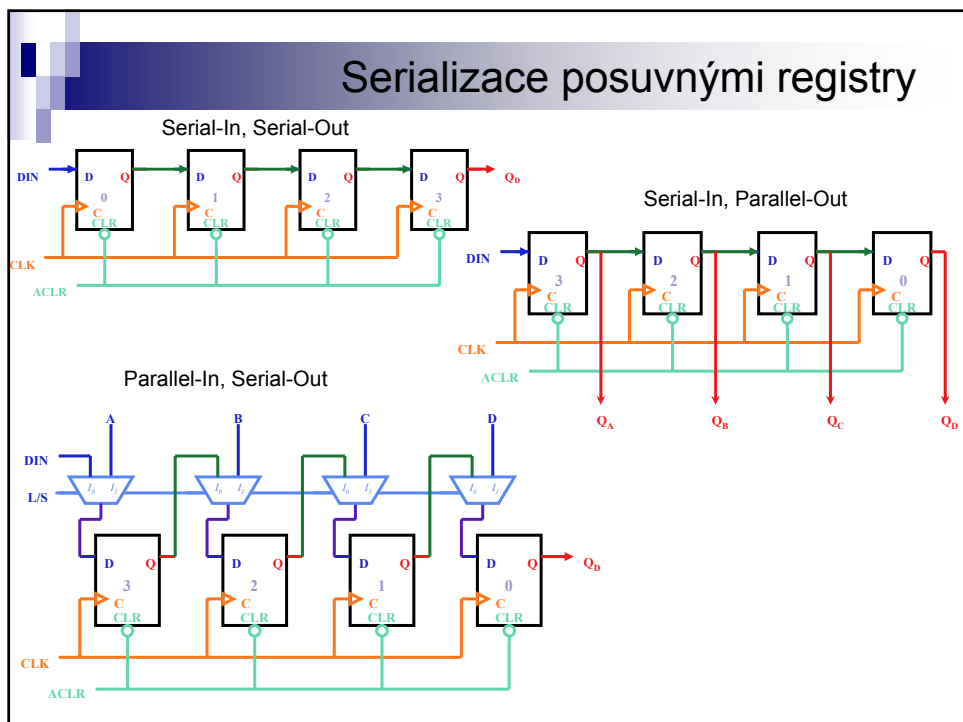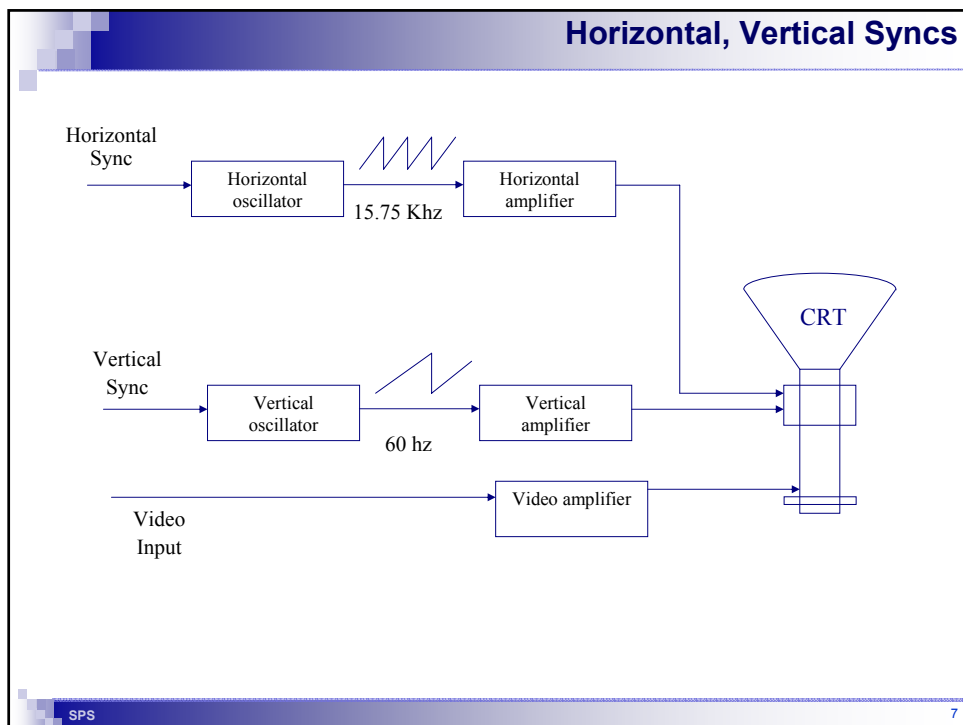

 Method-2:Shift Registers - CCD Readout 1/3



[Image source: Digital Photography Review]

SPS

9

Method-2:Shift Registers - CCD Readout 2/3

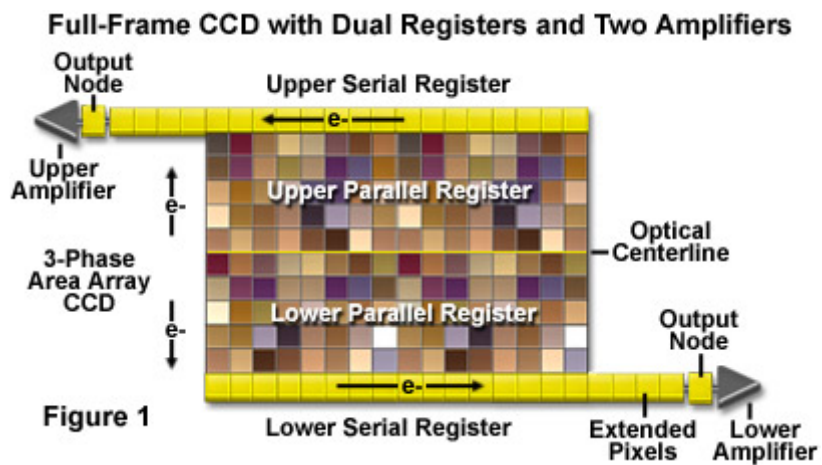


Figure 1


[Image source: Digital Photography Review]

SPS

10

Method-2: Shift Registers - CCD Readout 3/3

Standard CCD Readout Sequence


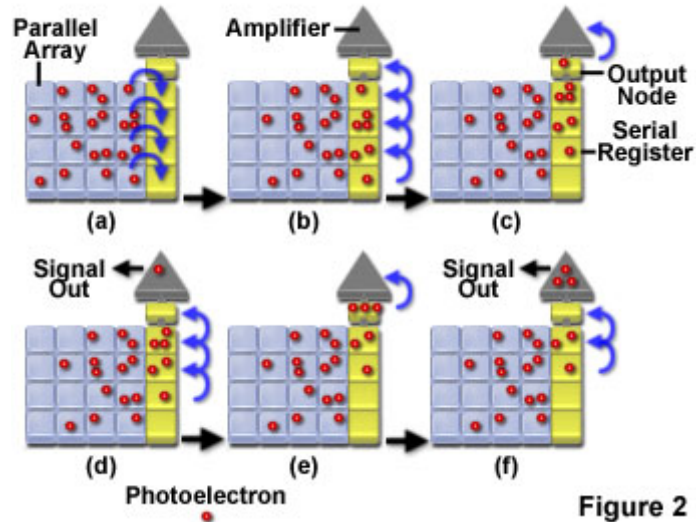


[Image source: Digital Photography Review]

SPS

11

Method-3: Row-Column

 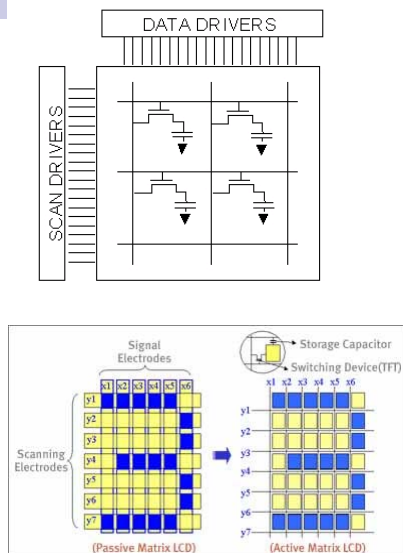

e.g. LCD matrices, memories



[Picture from: LCDs conceptos, Sony]



SPS

12

Introduced by IBM 1987

Video Graphic Array (VGA) Signal

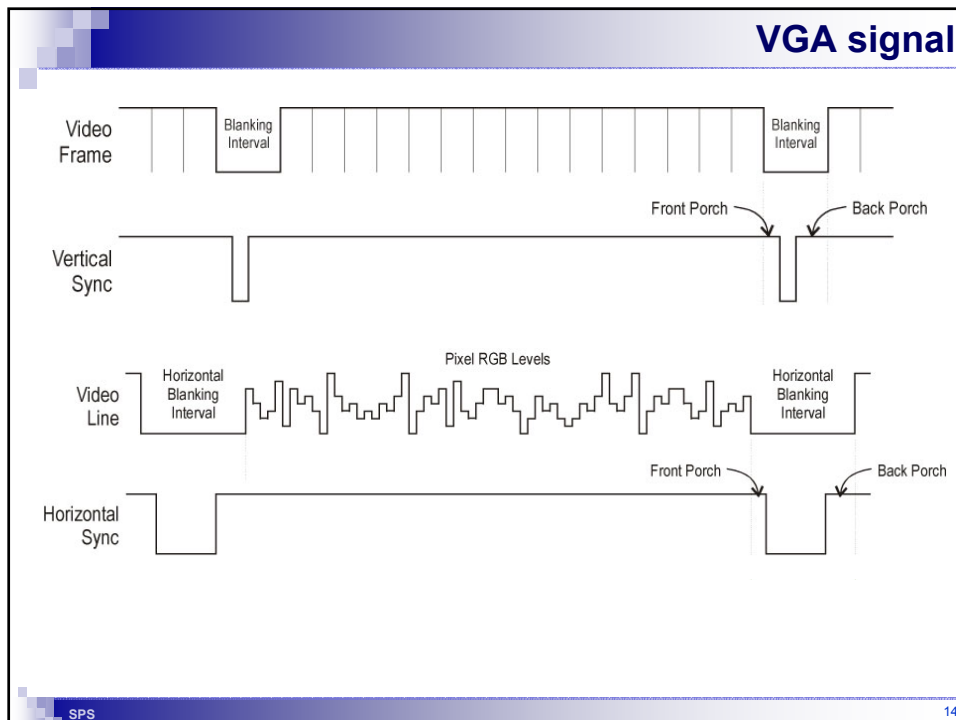 

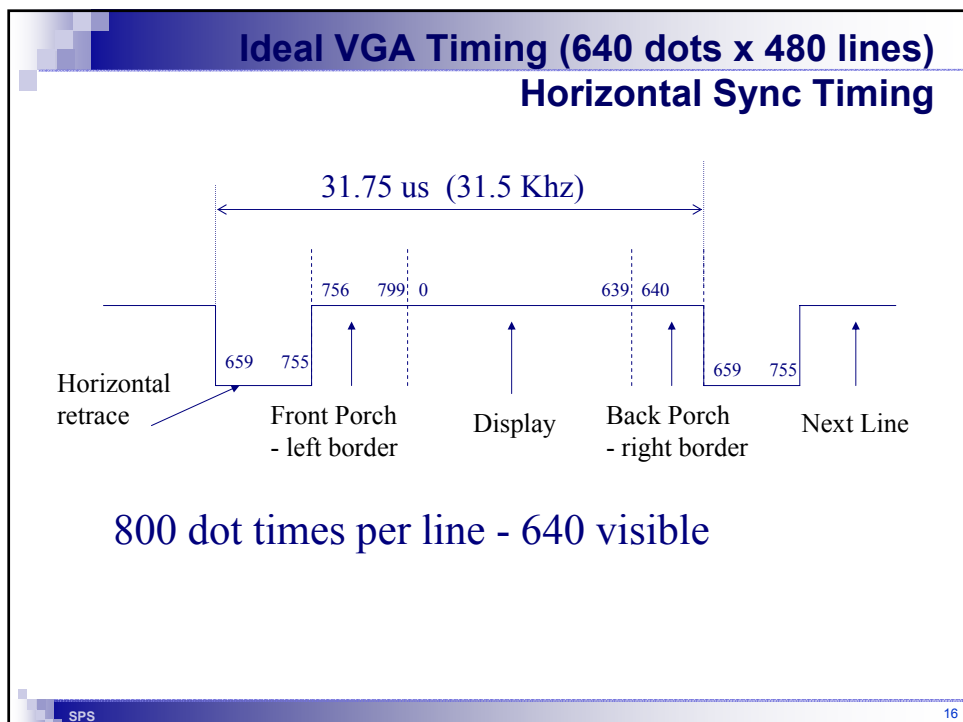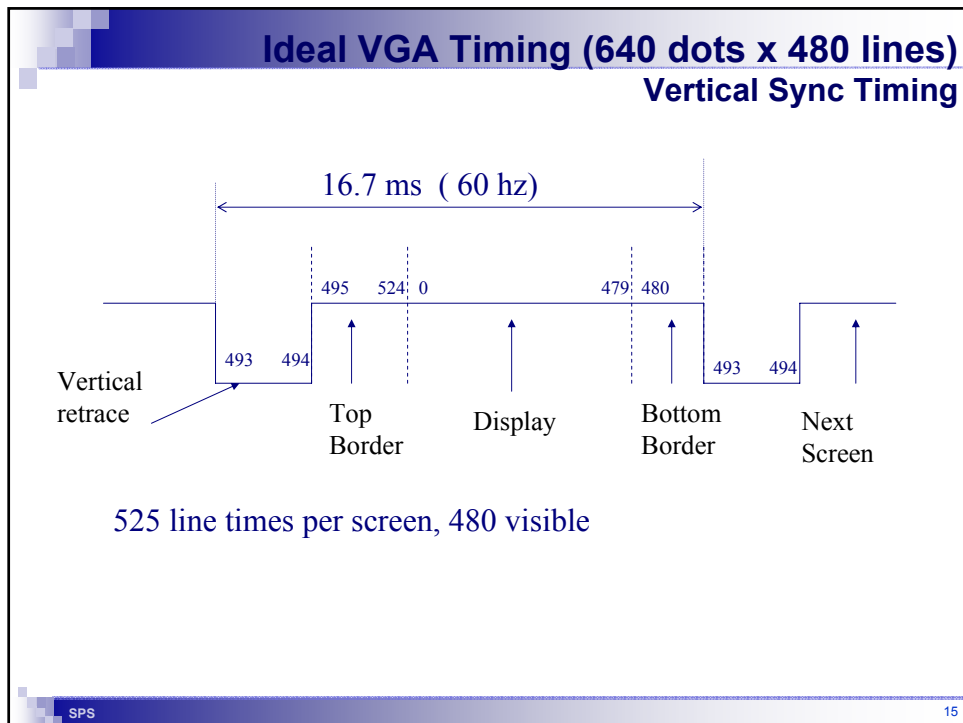

VGA					
VGA mode		Vertical Timing Spec			
Configuration	Resolution HxV	synchr. (lines)	front p. (lines)	frame (lines)	back p. (lines)
VGA(60Hz)	640x480	2	33	480	10
VGA(85Hz)	640x480	3	25	480	1
SVGA(60Hz)	800x600	4	23	600	1
SVGA(75Hz)	800x600	3	21	600	1
SVGA(85Hz)	800x600	3	27	600	1
XGA(60Hz)	1024x768	6	29	768	3
XGA(70Hz)	1024x768	6	29	768	3
XGA(85Hz)	1024x768	3	36	768	1
1280x1240(60Hz)	1280x1240	3	36	1024	1



SPS


17

DE2 - VGA							
Cz:Doporučená literatura: Jan Balcárek: Bakalářská práce, VUT Brno 2008 http://www.vutbr.cz/www_base/zav_prace_soubor_verejne.php?file_id=18649							
Video model		DE2					Standard
Configuration	Resolution HxV	synchr. (us).	front p. (us)l	row (us)	back p. (us)	Pixel clock (MHz)	Pixel clock
VGA(60Hz)	640x480	3,8	1,9	25,4	0,6	25	25,175
VGA(85Hz)	640x480	1,6	2,2	17,8	1,6	36	36
SVGA(60Hz)	800x600	3,2	2,2	20,0	1,0	40	40
SVGA(75Hz)	800x600	1,6	3,2	16,2	0,3	49	49,5
SVGA(85Hz)	800x600	1,1	2,7	14,2	0,6	56	56,25
XGA(60Hz)	1024x768	2,1	2,5	15,8	0,4	65	65
XGA(70Hz)	1024x768	1,8	1,9	13,7	0,3	75	75
XGA(85Hz)	1024x768	1,0	2,2	10,8	0,5	95	94,5
1280x1240(60Hz)	1280x1240	1,0	2,3	11,9	0,4	108	108
How to generate 25,175 a 36 MHz on DE2? - see the next lecture:-)							

SPS

18

 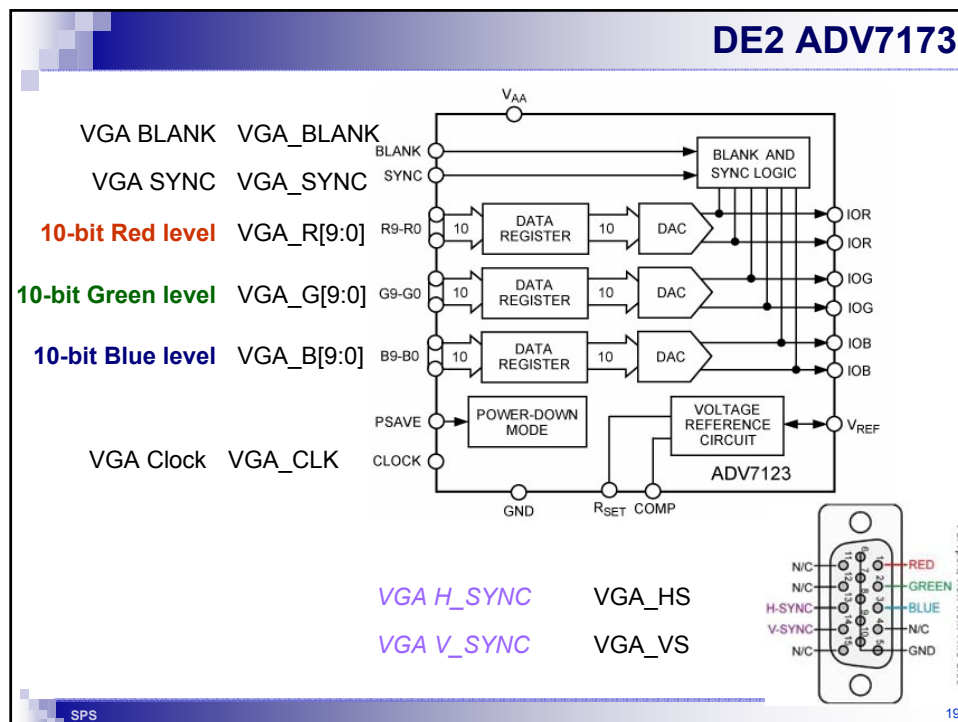

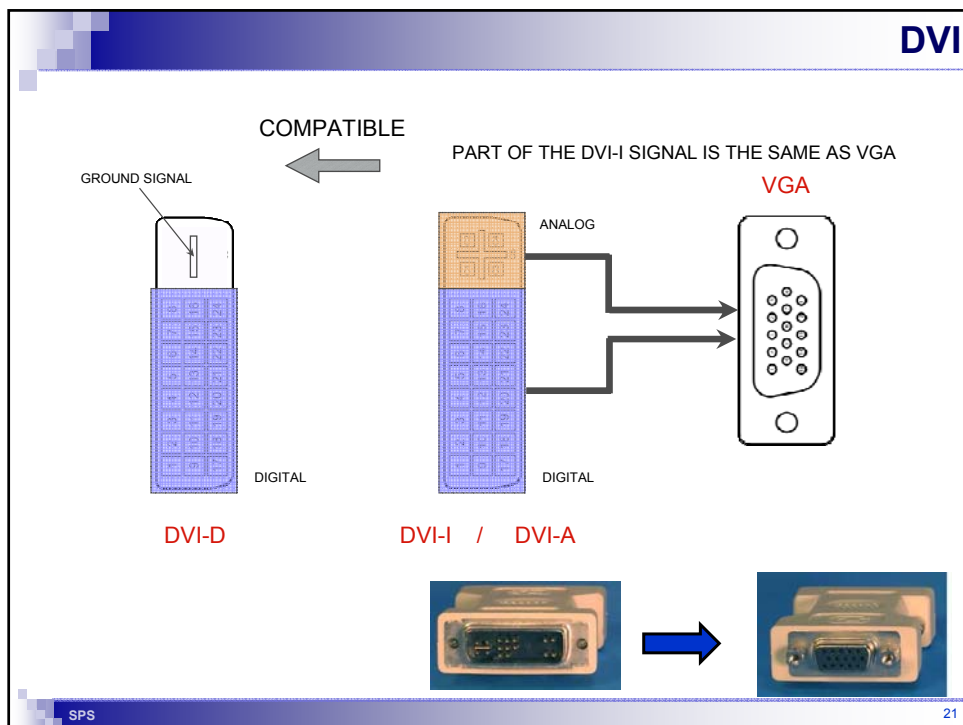

VHDL

jazyk logických obvodů

- Grafická schémata nedovolují snadno porovnávat verze návrhu, hledat změny
- **Hardware Description Language (HDL)**
 - Programovací jazyk pro modelování, simulaci a syntézu číslicových obvodů a systémů.
- Historie
 - 1980: US Department of Defense Very High Speed Integrated Circuit program (VHSIC)
 - 1987: Institute of Electrical and Electronics Engineers - IEEE Standard 1076 (VHDL'87)
 - 1993: VHDL revize a update
- **Verilog** - další významný HDL jazyk
 - podobný C, používaný hlavně v Americe a Japonsku
- Skoro všechny vývojové nástroje povolují Verilog i VHDL
- Programátoři obvodů se časem musí naučit oba jazyky
- **České firmy a školy používají primárně VHDL**

- *VHDL nerozlišuje malá a velká písmena*
- *Používané implementace většinou nerozumí česky, nelze tedy psát s diakritikou, a to ani komentáře.*
- *Silně typový jazyk s velmi omezenými implicitními konverzemi*
- *Silně upovídaný jazyk*
- *Silně neprogramátorský jazyk*
 - sestavili ho návrháři obvodů, nikoliv programátoři
 - píše se v stylem vhodným pro obvody a simulace
- *Každý obvod může být popsán pomocí VHDL a znovu použitý pro syntézu složitějších obvodů ve VHDL nebo symbolickém editoru*

Entity / Architecture

- Entity
 - Component interface
 - Inputs
 - Outputs

- Architecture
 - Structural
 - Non-procedural dataflow
 - Behavioral
 - Non-procedural dataflow
 - Procedural

text file (e.g., mydesign.vhd)

entity declaration

architecture definition

SPS
➡ 25

Terminologie

- Structural modeling
 - Komponenta je popsána svým složením z primitiv
- Behavioral modeling
 - Popisuje funkčnost, dynamické chování, ale neobsahuje implementaci...
 - ...překladač se pokusí najít možnou implementaci, výsledek bude
 - optimální / neoptimální / nelze zapojit ???
- Styl - Register Transfer Level – RTL
 - Styl návrhu v "behavior modeling"
 - Rozložení obvodu na menší jednotky
 - Používají se synchronní registry, hodiny...
 - ...při návrhu RTL myslíme v hardwaru.
 - Jedině RTL lze syntetizovat → vše ostatní se na RTL převádí

SPS
➡ 26


2-bit Comparator

$$\begin{aligned} \text{EQUALS} &= X1' . X0' . Y1' . Y0' + X1' . X0 . Y1' . Y0 \\ &\quad + X1 . X0' . Y1' . Y0 + X1 . X0 . Y1 . Y0 \\ &= LT' . GT' \end{aligned}$$

$$\text{LT: } X < Y = X1' . X0' . Y0 + X1' . Y1$$

$$\text{GT: } X > Y = X0 . Y1' . Y0' + X1 . Y1' + X1 . X0 . Y0'$$

Block Diagram

 

Y \ X	X1				
	00	01	11	10	
00	1	0	0	0	Y0
01	0	1	0	0	
11	0	0	1	0	
10	0	0	0	1	
X0					

K-map for EDUALS

Y \ X	X1				
	00	01	11	10	
00	0	0	0	0	Y0
01	1	0	0	0	
11	1	1	0	1	
10	1	1	0	0	
X0					


K-map for LT

Y \ X	X1				
	00	01	11	10	
00	0	1	1	1	Y0
01	0	0	1	1	
11	0	0	0	0	
10	0	0	1	0	
X0					

K-map for GT

Entity declaration

Define Input/Output (IO) pins

 

```

entity entity-name is
  port (signal-names : mode signal-type;
        signal-names : mode signal-type;
        ...
        signal-names : mode signal-type);
end entity-name;

```

*pozor, před) není už středník
jeho napsání je chybou!*

Entity defines IO pins

Case insensitive code!

Entity enclosed by the entity name –
eq2 (entered by the user)

```

entity eq2 is
  port (x1, x0, y1, y0: in std_logic;
        equals: out std_logic);
end eq2;


```



Port defines the I/O pins.

(Standard logic, an IEEE standard)

 4 inputs X0, X1, Y1, Y0 and 1 output EQUALS



VHDL: Multi-Valued Logic Representations

- Two popular signal representations exist:
 - MVL - 4
 - MVL - 9

MVL - 4			
Forcing 1	'1'	Forcing Unknown	'X'
Forcing 0	'0'	High Impedance	'Z'

31

Multi-Valued Logic Representations MVL - 9

more accurately states of signals

MVL - 9			
Unitialized	'U'	Weak 1	'H'
Don't Care	'-'	Weak 0	'L'
Forcing 1	'1'	Weak Unknown	'W'
Forcing 0	'0'	High Impedance	'Z'
Forcing Unknown	'X'		

} *Wired Or/And*


We will study wired or/and in some future lecture

32

Bit versus std_logic


- **Bit** - hodnoty '0' and '1'
- **Boolean** - hodnoty **TRUE** a **FALSE**
různé od bit, pouze pro podmínky,
- **std_logic MVL-9: - doporučeno**
'1', '0', 'X', 'Z', 'U', '-', 'L', 'H', 'W'
- **Pozor: std_logic a bit nelze vzájemně snadno převést**

4 typy IO signalů v deklaraci port

 

IN, OUT, INOUT, BUFFER modes

 - **IN**: data proudí pouze dovnitř - vstup
- **OUT**: data vystupují ven, pouze výstup.
Entita nemůže číst výstupy
- **INOUT**: obousměrný pro datové linky.
- **BUFFER**: podobný OUT, **ale entita smí číst zpět data**. Používáno pro adresy a řídicí signály CPU.




Modes of VHDL Ports

VHDL for programmable logic,
Skahill, Addison Wesley



Miniotázky: IN, OUT, INOUT, BUFFER


- Identifikujte módy IO pins ve schématu

 

VHDL for programmable logic,
Skahill, Addison Wesley



The architecture body

 

Define the internal
architecture/operation



Example of a Comparator


Entity declaration

```
entity eq2 is
  port (x1, x0, y1, y0: in std_logic;
        equals: out std_logic );
end eq2;
```



Architecture body
 
```
architecture dataflow1 of eq2 is
begin
  equals <= '1' when (x1 = y1) and (x0 = y0) else '0';
  -- "comment" equals is active high
end dataflow1;
```



```
architecture dataflow1 of eq2 is
begin
    equals <= '1' when (x1 = y1) and (x0 = y0) else '0';
    -- "comment" equals is active high
end dataflow1;
```

Operaci: `equals <= '1' when (x1 = y1) and (x0 = y0) else '0';`

čteme jako: *Equals pin gets value '1'*
 when (x1 = y1) and (x0 = y0)
 else it gets '0';

--" znamená komentář

equals, x1, x0, y1, y0 jsou "I/O signal pins"
 deklarované uživatelem

Relational Operators

- they have no relative precedences and
- their results has always type Boolean (TRUE,FALSE)

Symbol	Operator
=	Equal
/=	Not equal
<	Less than
<=	Less than or equal to
>	Greater than
>=	Greater than or equal to

```
equals <= '1' when (x1 = y1) and (x0 = y0) else '0';
```

Logical operators

defined for types: *boolean, std_logic, std_logic_vector*
and std_ulogic, std_ulogic_vector, bit, bit_vector

and *logical and*

or *logical or*

nand *logical complement of and*

nor *logical complement of or*

not *logical not*

xor *logical exclusive or*

xnor *logical complement of exclusive or*

equals <= '1' when (x1 = y1) **and** (x0 = y0) else '0';

41

„Concurrent“ Assignment

(cz:současné, souběžné)

Z <= not A;



Y <= A or B;

X <= C and D;

W <= E nor F;

V <= B nand D;

U <= C xor F;

  


equals <= '1' when (x1 = y1) **and** (x0 = y0) else '0';

42

Concurrent Assignments

Jaké přiřazení se provede dříve ve VHDL programu, to na prvním řádku, nebo na druhém řádku?

```
s <= a xor b;
c <= a and b;
```

 

- V implementaci: obě současně!
- **operace v hardwaru probíhají paralelně!**
- V simulaci: sice postupně, ale v nespecifikovaném pořadí
– **simulujeme hardware...**


equals <= '1' when (x1 = y1) and (x0 = y0) else '0';

SPS

43


Can the outputs be connected together?

Sometimes somewhere

 

Signal c1,c2, b1: std_logic;

~~b1 <= c1;~~
~~b1 <= c2;~~

 

Cyclon II and majority of other FPGA allow only one assignment each signal in program.

SPS

44

Conditional assignment

x-result must be specified for all possible cases

general form


⇒

```
x <=
  v1 when condition1 else
  v2 when condition2 else
  v3 when condition3 else
  ... else
  vN  -- all remaining cases
```

```
x <=
  (condition1 and v1) or
  (not condition1 and
   condition2 and v2) or
  (not condition1 and
   not condition2 and
   condition3 and v3) or
  ...
```

```
equals <= '1' when (x1 = y1) and (x0 = y0) else '0';
```

The architecture body

 

specifies used libraries

Library clause

```
library ieee;
use ieee.std_logic_1164.all;

entity eq2 is
    port (x1, x0, y1, y0: in std_logic;
          equals: out std_logic );
end eq2;

architecture dataflow1 of eq2 is
begin
    equals <= '1' when (x1 = y1) and (x0 = y0) else '0';
    -- "comment" equals is active high
end dataflow1;
```

SPS

47

Mini otázky

```
entity test1 is
    port (in1,in2: in bit;
          out1: out bit;
    end test1;
```

```
architecture test1arch of test1 is
begin
    out1<= in1 or in2;
end test1_arch;
```

Řekněte, které řádky obsahují deklaraci entity a které architekturu.

Nalezněte chybu v kódu.

Jaká je funkce deklarace a architektury u entity?

Nakreslete obvod se jmény pinů (pins).

Podtrhněte slova definovaná uživatelem v kódu nahoře.

SPS

48

Signál / sběrnice

- ☐ Signál dopravuje logickou informaci.
- ☐ Na úrovni hardwaru se realizuje vodičem (wire).
- ☐ Existuje mnoho druhů signálů dle přenášené informace
 - Std_logic = 1, 0, Z ..etc. (Z=vysoká impedance.)
 - Std_logic_vector - skupina signálů (wires) se nazývá „bus“ - sběrnice.



49

Vector Declarations

```
port (  
    A, B: in std_logic_vector(7 downto 0);  
    Z: out std_logic_vector(1 to 16)  
);
```

A, B:

7	6	5	4	3	2	1	0
---	---	---	---	---	---	---	---

Z:

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
---	---	---	---	---	---	---	---	---	----	----	----	----	----	----	----



SPS

50

STD_LOGIC_VECTOR

--Definition STD_LOGIC_VECTOR:

type STD_LOGIC_VECTOR

is array(NATURAL'RANGE <>) **of** STD_LOGIC;

-- NATURAL specifies numbers from 0 to n, where n depends on VHDL implementation

-- 'RANGE is attribute

-- <> means that the range of the type is unspecified (unconstrained)

subtype Natural **is** Integer **range** 0 **to** Integer'high;

subtype Positive **is** Integer **range** 1 **to** Integer'high;

*--Note: Arrays with different directions **to** or **downto** are mutually **inconvertible**!*

SPS

51

STD_LOGIC_VECTOR

SIGNAL x : std_logic_vector(31 **downto** 0);

SIGNAL y : std_logic_vector(0 **to** 31);

SIGNAL z1 : std_logic_vector(y'RANGE); *--(0 to 31)*

SIGNAL z2 : std_logic_vector(0 **to** y'LENGTH-1); *--(0 to 31)*

SIGNAL z3 : std_logic_vector(y'LOW **to** y'HIGH); *--(0 to 31)*

*--Note: Arrays with different directions **to** or **downto** are mutually **inconvertible**!*

SPS

52

Assignment Statements

```
SIGNAL x, y, z : STD_LOGIC;  
SIGNAL a, b, c : STD_LOGIC_VECTOR(7 DOWNT0 0);  
SIGNAL sel : STD_LOGIC_VECTOR(2 DOWNT0 0);
```

-- Concurrent Signal Assignment Statements

```
x <= y AND z; a <= b OR c;
```

-- Alternatively, signals may be assigned constants

```
x <= '0';  
y <= '1';  
z <= 'Z';  
a <= "00111010"; -- Assigns 0x3A to a  
b <= X"3A"; -- Assigns 0x3A to b  
c <= X"3" & X"A"; -- Assigns 0x3A to c  
sel <= a(5 DOWNT0 4) & '1';
```

SPS

53

EQ2 with Bus - cz:sběrnice

architecture dataflow2 of eq2 is

```
signal x,y:std_logic_vector(1 downto 0); -- internal signals
```

```
begin
```

```
    x <= x1&x0; y<= y1&y0; -- concatenate & by downto style  
    equals <= '1' when x=y else '0';
```

```
end dataflow2;
```

architecture dataflow3 of eq2 is

```
signal x,y:std_logic_vector(0 to 1); -- internal signals
```

```
begin
```


```
    x <= x0&x1; y<= y0&y1; -- concatenate & by to style  
    equals <= '1' when x=y else '0';
```

```
end dataflow3;
```

SPS

54

Entita a struktura VHDL souboru

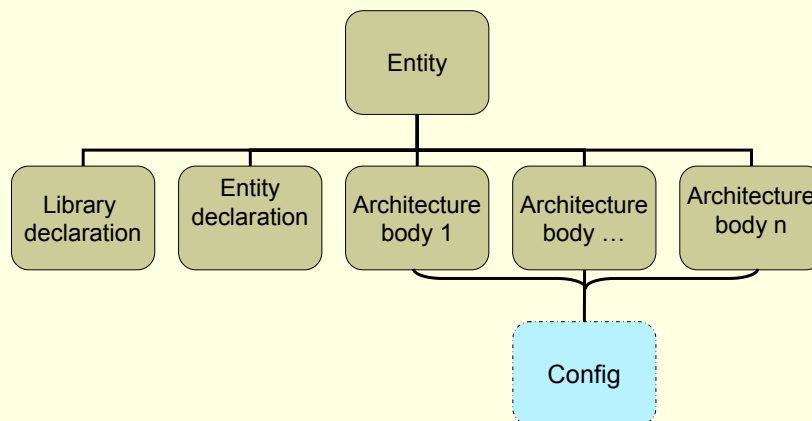

Configuration


```
configuration eq2config of eq2 is  
  for dataflow3  
  end for;  
end eq2config;
```

Entity – bus inputs

```
entity eq2bus is  
  port (x, y:   in std_logic_vector(1 downto 0);  
        equals: out std_logic);  
end eq2bus;
```



2 buses X, Y and 1 output EQUALS

 

EQ2BUS

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity eq2bus is  
  port (x, y: in std_logic_vector(1 downto 0);  
        equals: out std_logic );  
end eq2bus;  
  
architecture dataflow1 of eq2bus is  
begin  
  equals <= '1' when x=y else '0';  
end dataflow1;
```

EQGENERIC

```
library ieee;
use ieee.std_logic_1164.all;

entity eqGeneric is
  generic (
    DATA_WIDTH : natural := 8
  );
  port (x, y: in std_logic_vector(DATA_WIDTH-1 downto 0);
        equals: out std_logic );
end eqGeneric;

architecture dataflow1 of eqGeneric is
begin
  equals <= '1' when x=y else '0';
end dataflow1;
```

SPS

59

Full comparator with Generic

```
library ieee;
use ieee.std_logic_1164.all;

entity compGeneric is
  generic (DATA_WIDTH : natural := 8 );
  port (x, y: in std_logic_vector(DATA_WIDTH-1 downto 0);
        eq, lt, gt: out std_logic );
end compGeneric;

architecture dataflow1 of compGeneric is
begin
  eq <= '1' when x=y else '0';
  lt <= '1' when x<y else '0'; --how????
  gt <= '1' when x>y else '0'; --how????
end dataflow1;
```

SPS

60

AddGeneric



```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity addGeneric is  
  generic  
    (DATA_WIDTH : natural := 8  
    );  
  port (x, y: in std_logic_vector(DATA_WIDTH-1 downto 0);  
        z: in std_logic_vector(DATA_WIDTH-1 downto 0) );  
end addGeneric;  
  
architecture dataflow1 of addGeneric is  
begin  
  z<=x+y;  
end dataflow1;
```

SPS

61

Numbers in VHDL

Problem of Numeric
Representations

 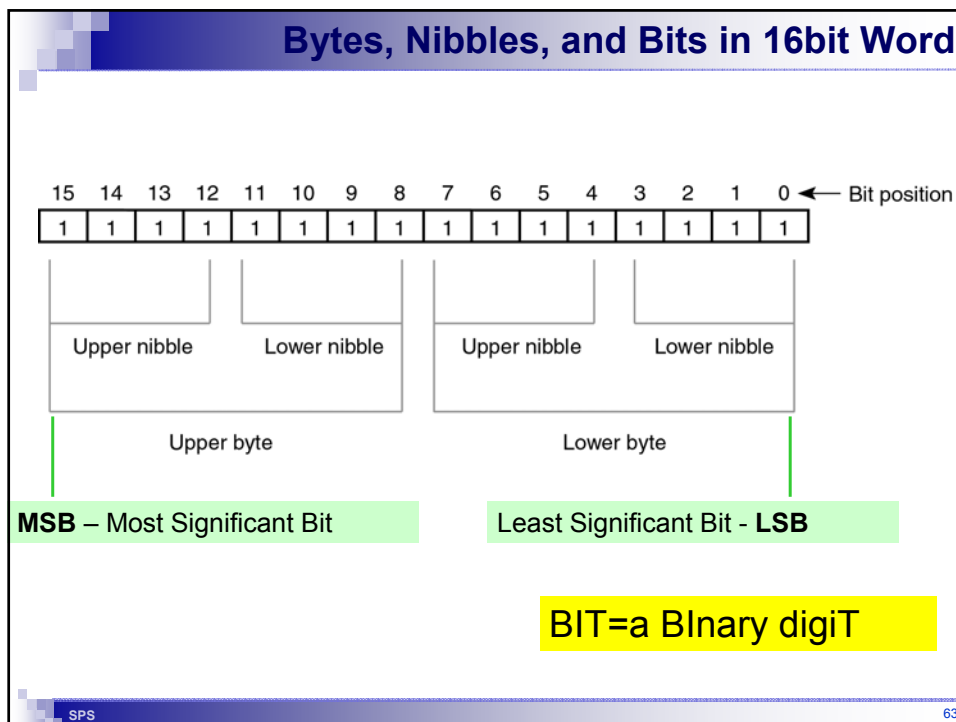

Two Ways of Storage in Memories

■ Hex Number: 1234567

Big Endian - *downto*

0x100	0x101	0x102	0x103
		01	23

Little Endian - *to*

0x100	0x101	0x102	0x103
		67	45



Pamatujete si, jak válka skončila?

SPS


65

Negative Number Systems

- Representation of positive numbers same in most systems, with exception Little/Big Endian storage
- **Major differences are in how negative numbers are represented** three major schemes:
 - sign and magnitude
 - ones complement
 - **twos complement**

Assumptions: we'll assume a 4 bit machine word

Unsigned 4-bit numbers

 


■ Cumbersome addition/subtraction

[Seungryoul Maeng: Digital Systems]

SPS

67

Sign and Magnitude Representation

 

■ Cumbersome addition/subtraction


■ Sign+Magnitude usually used only for float point numbers

[Seungryoul Maeng: Digital Systems]

SPS


68

 Ones Complement (In Czech: První doplněk)



- Still two representations of 0! This causes some problems
- Some complexities in addition

 Twos Complement (In Czech: Druhý doplněk)



- Only one representation for 0
- One more negative number than positive number

Poznámka: Bit versus std_logic v publikacích?

- **Bit** – hodnoty '0' and '1'
- **std_logic** MVL-9: '1', '0', 'X', 'Z', 'U', '-', 'L', 'H', 'W'
- **std_logic_arith** – verze pro aritmetické výpočty rozlišuje *signed / unsigned* – původně vyvinutá firmou Synopsys, čtyři různí výrobci si udělali nepatrně odlišné verze, později IEEE udělalo oficiální verzi of **std_logic_arith** called **numeric_std**
- **numeric_std** formální IEEE náhrada **std_logic_arith**
- nutno použít buď **std_logic_arith** nebo **numeric_std**, nikdy ne oboje!

SPS

71

Add STD_LOGIC_ARITH

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity addGeneric is
  generic
    ( DATA_WIDTH : natural := 8 );
  port (x, y: in std_logic_vector(DATA_WIDTH-1 downto 0);
        z: out std_logic_vector(DATA_WIDTH-1 downto 0) );
end addGeneric;

architecture dataflow1 of addGeneric is
begin
  z<=x+y;
end dataflow1;
```

SPS

72

```

library ieee;use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity unsigned_adder is
generic ( DATA_WIDTH : natural := 8 );
port ( a, b : in unsigned ((DATA_WIDTH-1) downto 0);
      result : out unsigned ((DATA_WIDTH-1) downto 0)
);
end entity;
architecture rtl of unsigned_adder is
begin result <= a + b;
end rtl;

```

SPS

73

Conversion functions

		numeric_std	std_logic_arith
Type Conversion			
std_logic_vector	-> unsigned	unsigned(arg)	unsigned(arg)
std_logic_vector	-> signed	signed(arg)	signed(arg)
unsigned	-> std_logic_vector	std_logic_vector(arg)	std_logic_vector(arg)
signed	-> std_logic_vector	std_logic_vector(arg)	std_logic_vector(arg)
integer	-> unsigned	to_unsigned(arg, size)	conv_unsigned(arg, size)
integer	-> signed	to_signed(arg, size)	conv_signed(arg, size)
unsigned	-> integer	to_integer(arg)	conv_integer(arg)
signed	-> integer	to_integer(arg)	conv_integer(arg)
integer	-> std_logic_vector	integer -> unsigned/signed -> std_logic_vector	
std_logic_vector	-> integer	std_logic_vector -> unsigned/signed -> integer	
unsigned + unsigned	-> std_logic_vector	std_logic_vector(arg1 + arg2)	arg1 + arg2
signed + signed	-> std_logic_vector	std_logic_vector(arg1 + arg2)	arg1 + arg2
Resizing			
unsigned		resize(arg, size)	conv_unsigned(arg, size)
signed		resize(arg, size)	conv_signed(arg, size)

From: <http://dz.ee.ethz.ch/support/ic/vhdl/vhdlsources.en.html>

SPS

74

Miniotázky : Nakreslete schéma obvodu

```
entity test is
  port (in1 : in std_logic_vector (2 downto 0);
        out1 : out std_logic_vector (3 downto 0));
end test;
architecture test_arch of test is
begin
  out1(0) <= in1(1);
  out1(1) <= in1(2);
  out1(2) <= in1(0) and in1(1);
  out1(3) <= '1';
end test_arch ;
```


*From VHDL for programmable logic,
Skahill, Addison Wesley*

SPS

75

Miniotázky: Napište entitu

 - Vyplňte pravdivostní tabulku a napište VHDL kód



In1	in2	out0	out1	out1	out0
		0	0	1	1

*From VHDL for programmable logic,
Skahill, Addison Wesley*

SPS

76

Příklady

VHDL kompinační obvody

Dekodér

Příklad: 2-to-4 dekodér

```


entity decoder is
  port (
    A : in std_logic_vector(1 downto 0);
    Z : out std_logic_vector(3 downto 0)
  );
end entity decoder;

architecture when_else of decoder is
begin
  Z <= "0001" when A = "00" else
        "0010" when A = "01" else
        "0100" when A = "10" else
        "1000" when A = "11" else
        "XXXX";
end architecture when_else;

```

Interface

Functionality

 

A(1..0)		Z(3..0)			
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

VHDL for programmable logic, Skahill, Addison Wesley

Decoder for 7-segment display

SPS

79

BCD / 7-segment

A	B	C	D	c0	c1	c2	c3	c4	c5	c6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

SPS

80

7segment Entity

```
entity entity-name is
  port (signal-names : mode signal-type;
        signal-names : mode signal-type;
        ...
        signal-names : mode signal-type);
end entity-name;
```

LIBRARY ieee;

USE ieee.std_logic_1164.**ALL**;

-- 7segment driver hex display of a number

ENTITY SevenSegment **IS**

PORT(D, C, B, A :**IN** STD_LOGIC;

segmentsOut: **OUT** STD_LOGIC_VECTOR(6 **DOWNTO** 0)
);

END SevenSegment;


SPS

81

Conditional Signal Assignment

```
c <= "0" when a /= b else
      "1" when a = '1' else
      b;
```

means

 

SPS


82

Selected Signal Assignment

with x select

```
c <= "0" when "00" ,
      "1" when "01" | "10" ,
      "b" when others;
```

means

 

- Resulting circuit is more compact and faster than circuit produced by conditional assignment.

Assignment Statements (summary)

```
SIGNAL x, y, z :STD_LOGIC;
SIGNAL a, b, c :STD_LOGIC_VECTOR( 7 DOWNTO 0);
SIGNAL sel :STD_LOGIC_VECTOR( 2 DOWNTO 0);
```

-- Conditional Assignment Statement

```
x <='0' WHEN sel = "000" ELSE
y      WHEN sel = "011" ELSE
z      WHEN x = '1' ELSE
'1';
```

-- Selected Signal Assignment Statement

-- NOTE: The selection values must be constants

```
WITH sel SELECT
x <= '0' WHEN "000",
y    WHEN "011",
z    WHEN "100",
'1'  WHEN OTHERS;
```

-- Selected signal assignments also work with vectors

```
WITH x SELECT
a <= "01010101" WHEN '1',
b  WHEN OTHERS;
```

7segment ARCHITECTURE

```

architecture Behavioral of SevenSegment IS
Signal dataIn:STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN dataIn <= D & C & B & A; -- concatenate operator (&)
with dataIn SELECT-- LSB is A
    segmentsOut <="1000000" WHEN "0000",-- 0
                "1111001" WHEN "0001",-- 1
                "0100100" WHEN "0010", -- 2
                "0110000" WHEN "0011", -- 3
                "0011001" WHEN "0100",-- 4
                --
                --
                "0000011" WHEN "1011",-- b
                "0100111" WHEN "1100",-- c
                "0100001" WHEN "1101",-- d
                "0000110" WHEN "1110",-- E
                "0001110" WHEN others;-- for F "111" and simulation

END Behavioral;

```

SPS

85

7segment with ripple blanIn / blankOut

```

ENTITY SevenSegment IS
    PORT( D, C, B, A :IN STD_LOGIC; blankIn :IN STD_LOGIC;
          blankOut : OUT STD_logic;
          segmentsOut: OUT STD_LOGIC_VECTOR(6 DOWNTO 0) );
END SevenSegment;

architecture Behavioral of SevenSegment IS
Signal dataIn:STD_LOGIC_VECTOR(3 DOWNTO 0);
Signal segments: STD_LOGIC_VECTOR(6 DOWNTO 0);
BEGIN
    dataIn <= D & C & B & A;
    with dataIn SELECT-- LSB is A
        segments <="1000000" WHEN "0000",-- 0
                "1111001" WHEN "0001",-- 1
                "0100100" WHEN "0010", -- 2
                --
                --
                "0000110" WHEN "1110",-- E
                "0001110" WHEN others;-- for F "111" and simulation

    blankOut <= '1' when dataIn="0000" and blankIn='1' else '0';
    segmentsOut <= segments when dataIn /= "0000" or blankIn='0' else "1111111"

END Behavioral;

```

SPS

86

...KONEC...
a nashledanou příště

